

Arduino + 4 pin 5mm Full-Color

LED

Written By: Danny Pena




 Computer running Windows, OSX or Linux (1)

PARTS:

- Transistor, NPN (3)
- Resistor (3)
- 5mm Full-Color LED (1)
- Jumper Wire Pack (1)
- Arduino (1)
- Breadboard (1)

Step 1 — Schematic

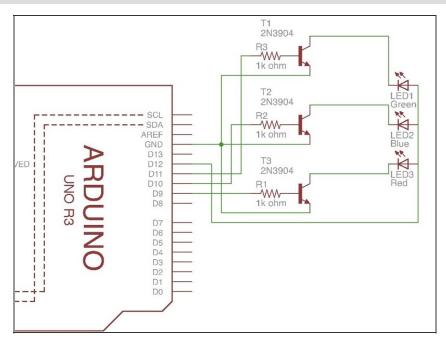



 This circuit uses an Arduino UNO but it still works on an Arduino MEGA 2560.



• In this project we only use one 5mm LED, but since the LED has four pins, I used three LED symbols in place of the fourpin LED. The three cathodes of the LEDs in the schematic are the three cathodes on the Full-Color 5mm LED. The three anodes of the LEDs are the one anode on the Full-Color 5mm LED.

Step 2

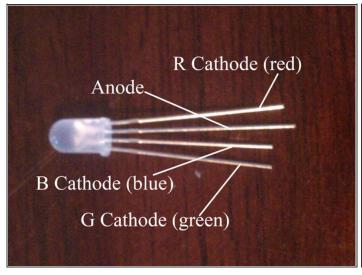

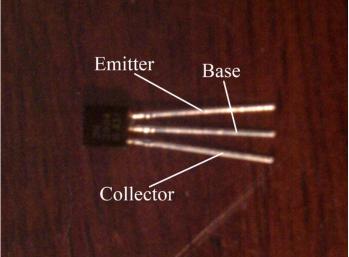

- Remember, the longest pin of the LED is the anode, the other three short pins are the cathodes (RGB)
- Also, while the flat side of the transistor is facing you, the left pin is the collector, the middle is the base, and the right pin is the emitter.



 The photo notes the 2N2222 transistor. For the 2N3904 and 2N4401, the Collector and Emitter are switched.




Step 3 — Circuit Assembly



- Connect the LED to the breadboard.
- Connect the anode of the LED to the other half of the breadboard.
- Connect the cathode (frist pin) to the other side of the breadboard.

Step 4 — **LED to Transistor**

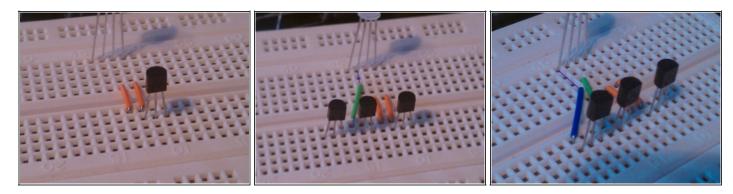

- Connect the collector of one transistor to the first cathode of the LED.
- Connect the other transistors as shown in the image. Connect the collector of the second transistor to the second cathode of the LED.
- Connect the collector of the third transistor to the third cathode of the LED.
- I'm using the 2N2222 transistor, so in my case the transistor faces my direction. If the 2N3904 or 2N4401 transistor are used, the transistor will face the opposite direction.




Step 5 — **Transistor to Resistor**




- Connect one resistor to the base of the third transistor.
- Connect the second resistor to the base of the second transistor.
- Connect the third resistor to the base of the first transistor.

Step 6 — **Transistor to Ground**

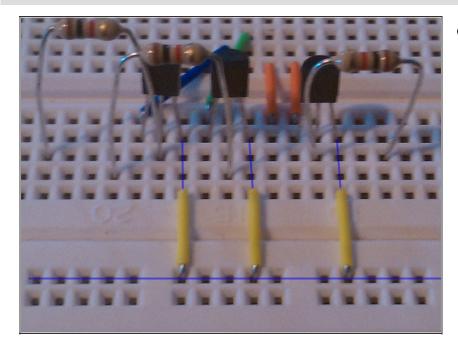


 Connect the emitter of all three transistors to ground.

Step 7 — **Resistor to Arduino**

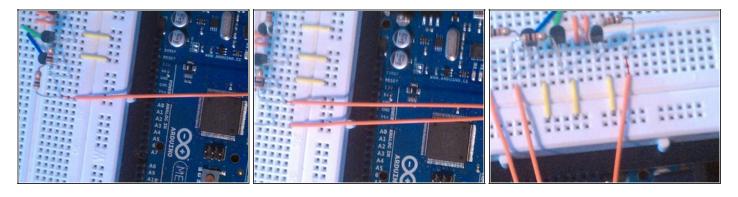

- Connect the resistor from the third transistor to pin 9 on the Arduino.
- Connect the resistor from the second transistor to pin 10 on the Arduino.
- Connect the resistor from the first transistor to pin 11 on the Arduino.

Step 8 — Ground and LED anode to Arduino

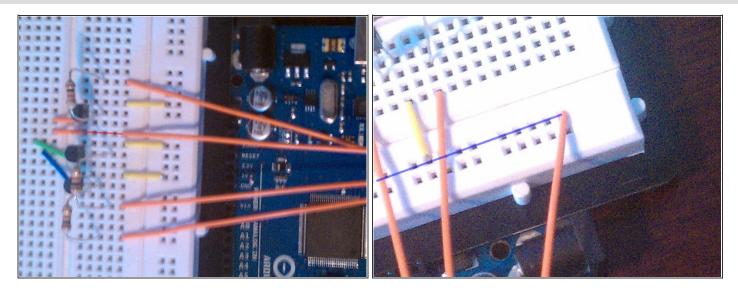


- Connect the anode of the LED to pin 12 on the Arduino.
- Connect ground from the Arduino to the ground strip of the breadboard.

Step 9 — Arduino Program

```
// you now indexion that the power for the choice on the LED int lead = $11 // pin 12 is the power for the choice on the LED int lead = $11 // pin 12 is for the (plus) 8 catchode of the LED int lead = $11 // pin 12 is for the (plus) 8 catchode of the LED int lead = $11 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the (plus) 8 catchode of the LED int lead = $1 // pin 12 is for the plus interview (plus) 8 catchode into plus interview (plus) 8 catchod
```


- Connect your Arduino to your computer (running Windows, OSX, Linux).
- Open the Arduino program and upload the Arduino code within the following images.

Step 10 — Arduino Serial Monitor Testing

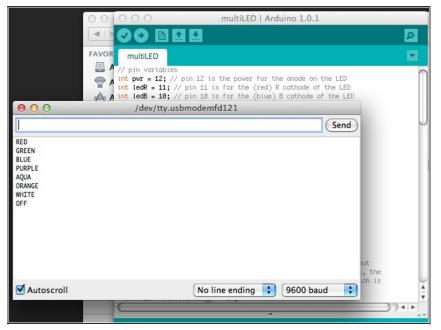


- After uploading the code, open the serial monitor and input a character from 1 - 8.
 - 1 = RED, 2 = GREEN, 3 = BLUE
 - The LED only has three pins for RGB (Red, Green, Blue), but turning on more then one pin creates diverse colors.
 - 4 = PURPLE, 5 = AQUA, 6 = ORANGE, 7 = BRIGHT WHITISH PURPLE
 - 8 = OFF

Step 11 — RGB colors

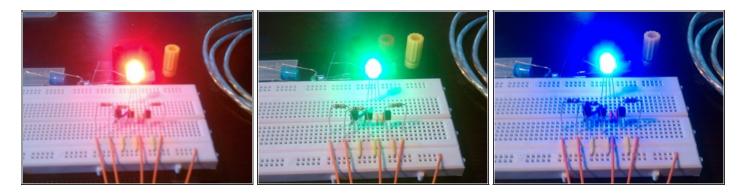


Normal RGB light settings.

Step 12 — RB, GB, and RG colors

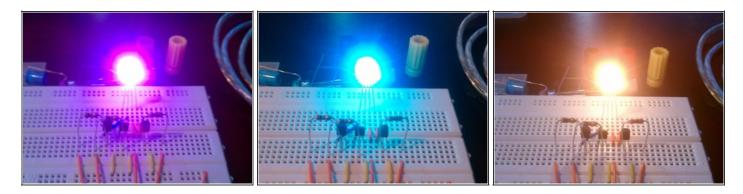

• Other RGB settings. RB, GB, or RG.

Step 13 — LED all on or off

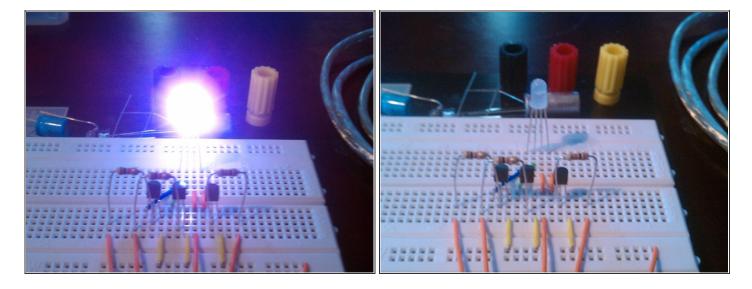

All RGB cathodes on or off.

This document was last generated on 2012-10-31 04:40:25 AM.